
ECE 551 Exercise 7

Spring '18

March 16 Due March 21, 11:00am

MAC module

 

| Signal | Dir. | Wid. | Description |
|--------|------|------|---------------------|
| a | I | 8 | Operand A (signed) |
| b | I | 8 | Operand A (signed) |
| of | O | 1 | Overflow indicator |
| uf | O | 1 | Underflow indicator |
| clr_n | I | 1 | Clear (active low) |
| acc | O | 16 | Accumulator output |

- Signed 8-bit MAC module
- Use dataflow Verilog for the datapath
- Use behavioral Verilog only for the registers
- clk and rst_n are implicit

Overflow and underflow

- Sign extend the input by 1 bit
 - e.g., $+7 = 0111 \rightarrow 00111$, $+1 = 0001 \rightarrow 00001$
 - e.g., $-8 = 1000 \rightarrow \underline{1}1000$, $-1 = 1111 \rightarrow \underline{1}1111$
- Add
- Compare 2 MSBs
 - 01 = Overflow
 - e.g., 7 + 1 = 00111 + 00001 = 01000 = 8. Overflow occurs since 8 cannot be represented in 4 bits.
 - 10 = Underflow
 - e.g., -8 1 = 11000 + 11111 = 10111 = -9. Underflow occurs -9 cannot be represented in 4 bits.
 - Otherwise, no over/underflow.

Testbench

- Write a testbench that keeps monitoring of and uf and display a message if any detected
 - No need to display any message if no of/uf detected
- Calculate the following:
 2*5 + (-2)*5 + (-3)*8
 - Does an overflow or underflow occurs?
- Calculate the following:
 126*126 + 126*126 + 126*126
 - Does an overflow or underflow occurs?
- Write an example that generates an underflow

Submit

- mac.sv
- mac_tb.sv exercising the MAC with the three input pairs
- screenshot.png showing one overflow and one underflow case

Team formation

- Make a team of 4 by noon Wednesday 3/21
- Register at https://goo.gl/forms/bpXPNHNtfywqrcYq2
- Let me know if you fail to make a team of 4
 - We have 78 students. One of the current teams of 2 should be split and make two teams of 3.
 - Teams of 3 get a small extra credit.